



GOVERNMENT COLLEGE OF ENGINEERING, JALGAON

(An Autonomous Institute of Government of Maharashtra)

National Highway No.6, JALGAON – 425 002

Phone No.: 0257-2281522

Fax No.: 0257-2281319

Website : www.gcoej.ac.in

E-mail : princoej@rediffmail.com



Name of Examination : **Winter 2020** - (Preview)

Course Code & Course Name : **IN201U - Analog Electronics**

Generated At : **19-04-2022 10:36:28**

Maximum Marks : **60**

Duration : **3 Hrs**

[Edit](#) [Print](#) [View Answer Key](#) [Close](#) **Answer Key Submission Type:** Marking scheme with model answers and solutions of numerical

Instructions:

- All questions are compulsory.
- Illustrate your answer with suitable figures/sketches wherever necessary.
- Assume suitable additional data; if required.
- Use of logarithmic table, drawing instruments and non programmable calculators is allowed.
- Figures to the right indicate full marks.

1) Solve any three sub-questions.


- Discuss the behaviour of p-n junction diode under forward and reverse biased conditions. [5]
- What is Clamper Circuit? Classify and explain Clamper. [5]
- Calculate the reverse saturation current of a diode if the current at 0.2V forward bias is 0.1mA at a temperature of 25°C and the ideality factor is 1.5. [5]
- Compare CE,CC and CB configurations. [5]

2) Solve any three sub-questions.

- Draw the circuit diagram of a voltage divider bias and derive expression for Stability factor. [5]
- Draw the circuit diagram of a push-pull amplifier. Explain its operation. Discuss advantages and disadvantages. [5]
- Explain working of Class A amplifier. state its applications. [5]
- Explain the Input and output characteristics of transistor in Common Base Configuration. [5]

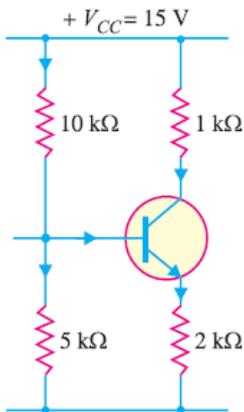3) Solve any three sub-questions.

- Describe the construction and working principle of Enhancement mode and depletion mode MOSFET and draw its characteristics. [5]
- Figure shows the voltage divider bias method. Draw the d.c. load line and determine the operating point. Assume the transistor to be of silicon [5]



- Draw the small signal model of FET. Compare it with model of BJT. [5]
 - State advantages of Negative feedback in amplifiers. [5]
- 4) a) Discuss biasing of Enhancement MOSFET. Derive equation for Drain current. [5]
- b) **Write note on** [10]
- Hartley Oscillator.
 - Photodiode.

Auto Generated by SsOES v6.2