


**GOVERNMENT COLLEGE OF ENGINEERING, JALGAON**

(An Autonomous Institute of Government of Maharashtra)

National Highway No.6, JALGAON – 425 002

Phone No.: 0257-2281522

Fax No.: 0257-2281319

Website : www.gcoej.ac.in

E-mail : princoej@rediffmail.com


 Name of Examination : **Winter 2020** - (Preview)

 Course Code & Course Name : **EE101U - Elements of Electrical Engineering**

 Generated At : **19-04-2022 10:33:25**

 Maximum Marks : **60**

 Duration : **3 Hrs**
[Edit](#) [Print](#) [View Answer Key](#) [Close](#) **Answer Key Submission Type:** Marking scheme with model answers and solutions of numerical

Instructions:

1. All questions are compulsory.
2. Illustrate your answer with suitable figures/sketches wherever necessary.
3. Assume suitable additional data; if required.
4. Use of logarithmic table, drawing instruments and non programmable calculators is allowed.
5. Figures to the right indicate full marks.

**1) Solve any three sub-questions.**

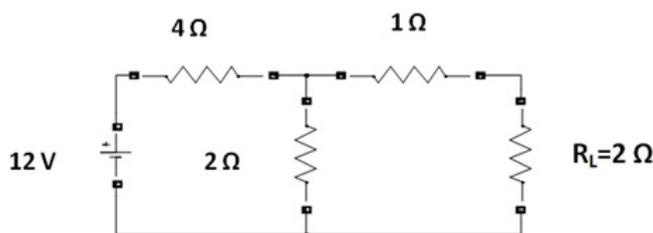
 a) Compute the current flowing through load resistor  $R_L$  in given figure No.1 [4]


Figure No.1

 b) What do you understand by DC sources? Explain source conversion with suitable example. [4]

 c) Derive an expression for the instantaneous current through pure inductance alone, when sinusoidal single phase voltage is applied. [4]

 d) Describe power and impedance triangle and explain the terms active power, reactive power and power factor. [4]
**2) Solve any three sub-questions**

 a) Two impedance  $Z_1=2+j6$  and  $Z_2=6-j12$  are connected in series. If 100 volt is connected, find the resultant impedance and current in rectangular and polar form. [4]

 b) A coil of resistance  $12\Omega$  and inductive reactance of  $25\Omega$  is connected in series with a capacitive reactance of  $14\Omega$ . The combination is connected to supply of 230 volt, 50 Hz. Find (i) Impedance (ii) Current and (iii) power consumed by circuit. [4]

 c) What do you understand by balance load? Derive and state the relation between Phase and line values of voltage and current for star connected load [4]

 d) Prove that average power consumption in pure inductor is zero when a.c voltage is applied. [4]
**3) Solve all sub-questions**

 a) What is meant by hysteresis and eddy current losses in magnetic materials? [6]

 b) Compare electric and magnetic circuit by their similarities and dissimilarities. [6]
**4) Solve any two sub-questions**

 a) Show that voltage ratio of primary and secondary winding of transformer is same as their turns ratio. [6]

 b) Describe voltage regulation of transformer. Comments on voltage regulation value based on nature of load. [6]

 c) Explain construction and working operation of three phase induction motor. State advantages over single phase motor. [6]
**5) Solve any three sub-questions**

 a) Develop the phasor diagram of single phase transformer under load condition. Assume lagging power factor load. [4]

 b) State best safety practices and safety measure in electrical works. [4]

 c) What is the need of earthing in electrical installation? Explain with suitable example [4]

 d) Differentiate between Miniature Circuit Breaker (MCB) and Earth Leakage Circuit Breaker (ELCB). State application [4]

Auto Generated by SsOES v6.2